

Name: _____ ID# _____

Date Submitted: _____ Lab Section # _____

CSE 2441 – Introduction to Digital Logic

Fall Semester 2014

Lab Number 4 – Introduction to the Altera DE1

100 Points

To be performed September 25-26, 2014

INTRODUCTION TO THE ALTERA DE1 DEVELOPMENT AND EDUCATION BOARD

(100 POINTS)

PURPOSE and OUTCOME: To give you experience using the basic features of the DE1 and programming the on-board Cyclone II field programmable gate array (FPGA). Once you've successfully completed the exercises below, you will be able to implement and test basic digital logic circuits on the DE1.

BASIC DE1 FEATURES

The DE1 Development and Education Board is suitable for use in undergraduate teaching laboratories, yet it is powerful enough for prototyping of complex designs. An image of the DE1 is shown below in Figure 1. Features of the DE1 include the following.

- Cyclone II EP2C20F484C7 field programmable gate array
- Ten data switches (SW0-SW9)
- Four debounced pushbutton switches (KEY0-KEY3)
- Ten red LED displays (LEDR0-LEDR9)
- Eight green LED displays (LEDG0-LEDG7)
- Four 7-segment LED displays (HEX0-HEX3)
- RUN/PROG switch
- ON/OFF switch
- Power port
- USB/MIC/LINE-IN/LINE-OUT/VGA/RS-232/PS2/BNC I/O ports
- Two header blocks
- SD memory card slot
- SDRAM/SRAM/Flash on-board memory chips

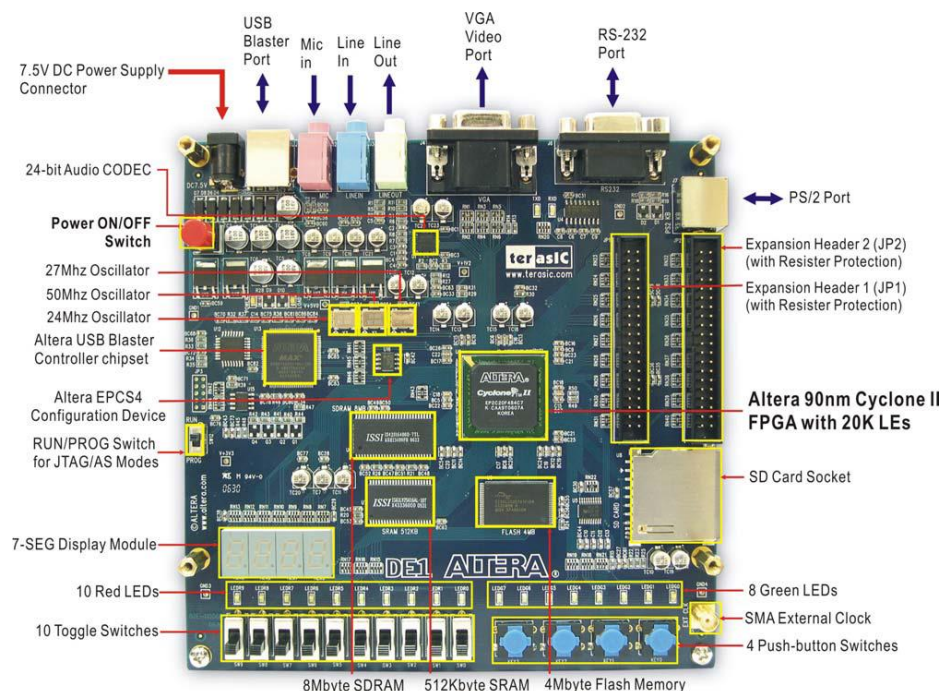


Figure 1. DE1 Layout.

BASIC OPERATION AND PROGRAMMING OF THE DE1

Run the Power-On test that is preprogrammed in to the on-board Cyclone II FPGA.

1. Plug the power supply in to an AC outlet and then in to the DE1 power port.
2. Connect the DE1 to your laboratory computer using a USB cable.
3. Place the RUN/PROM switch in the RUN position.
4. Press the red Power button to turn on the DE1.
5. A correctly functioning DE1 will now be displaying the following.
 - Blue Power LED will be on
 - The hexadecimal characters will be cycling over and over on the 7-segment displays
 - The red and green LEDs will be flashing.

This test will run every time the DE1 is powered on unless the test program has been erased.

The Cyclone II FPGA must be configured or “programmed” before it can perform or implement the desired functionality. Programming an FPGA is the equivalent of interconnecting gates and flip flops with wires or a printed circuit. But, as you will learn, much easier and faster.

Programming the Cyclone II is done using tools provided in Quartus II. So programming is an extension of the design flow that you’ve been following in previous exercises as follows.

1. Capture, or enter, your circuit design using Quartus II. This can be a circuit diagram or HDL (VHDL or Verilog) code.
2. Compile your design.
3. Verify your design using Qsim or another simulator.
4. Assign the input/output nodes of your design to specific pins on the FPGA. This can be done using the Quartus II Assignment Editor.
5. Recompile your design so that the input/output assignments will be incorporated.
6. Download or program the Cyclone II with your design using the Quartus II Programmer tool.
7. Test your design using the DE1 input switches and output LEDs.

USING THE DE1 – GUIDED TOUR

In this section, you will be guided through these steps for the circuit shown below in Figure 2. You may recognize that this is the same circuit that you captured in Laboratory Exercise 2 when learning to use Quartus II.

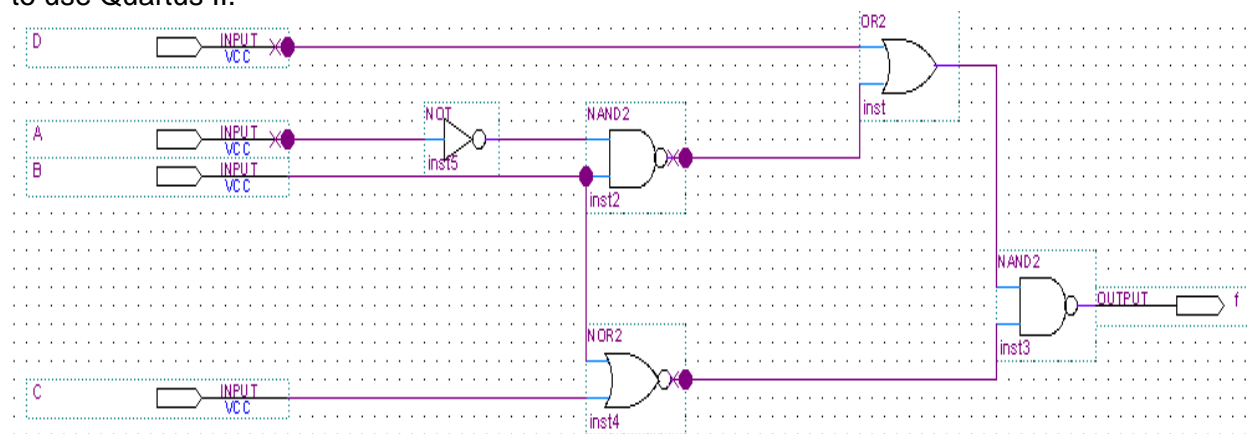



Figure 2. DE1 Guided Tour Exercise Schematic Diagram.

1. Capture the circuit schematic using Quartus II or reuse your .bdf file from lab2. Make sure that the Cyclone II family and EP2C20F484C7 device have been selected.
2. Compile your design.
3. Verify your design using Qsim.
4. The circuit inputs A,B,C,D and output f must be assigned to specific switches and LEDs on the DE-1 in order for the Programmer to properly make the connections to the Cyclone II FPGA device. Use the assignments below for this design. See appendix A for the pin assignments for all of the DE-1 I/O switches and LEDs.

A (SW3) -> PIN_V12	Aout (LEDR3) -> PIN_Y19
B (SW2) -> PIN_M22	Bout (LEDR2) -> PIN_U19
C (SW1) -> PIN_L21	Cout (LEDR1) -> PIN_R19
D (SW0) -> PIN_L22	Dout (LEDR0) -> PIN_R20
f (LEDG0) -> PIN_U22	


Use the Quartus II Assignments Editor to enter the assignments as illustrated below.

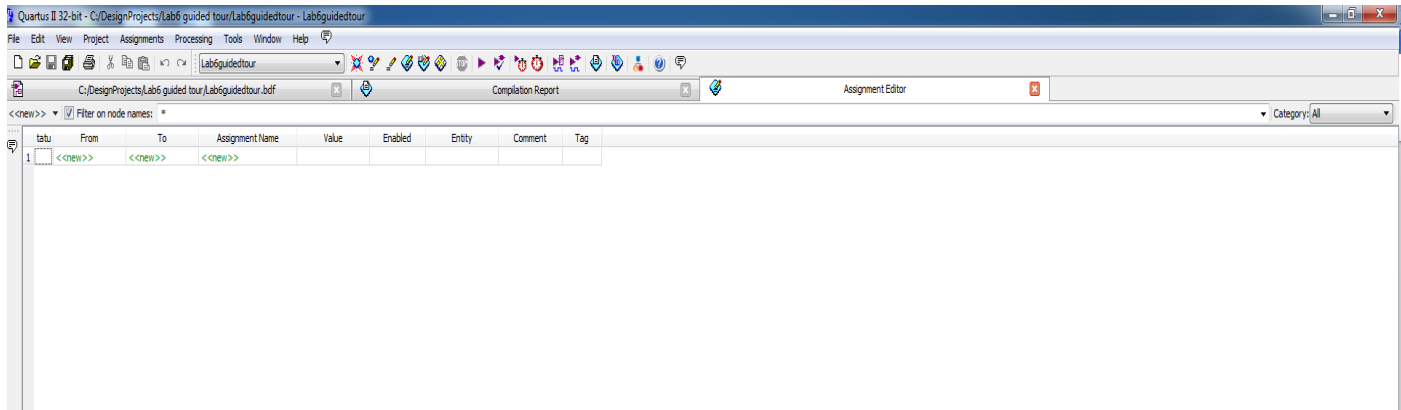Select **Assignments > Assignment Editor** from the Quartus II menu which will take you to the following window.




All should be selected in the **Category** drop-down menu.

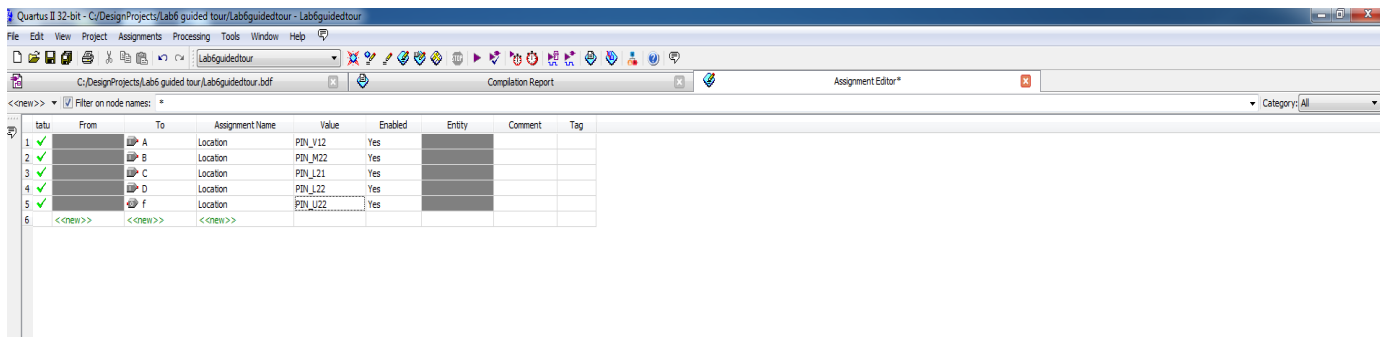Now enter the pin assignments by filling the **To**, **Assignment Value**, and **Value** columns. This will produce the following window. Save the assignment using **File > Save**.




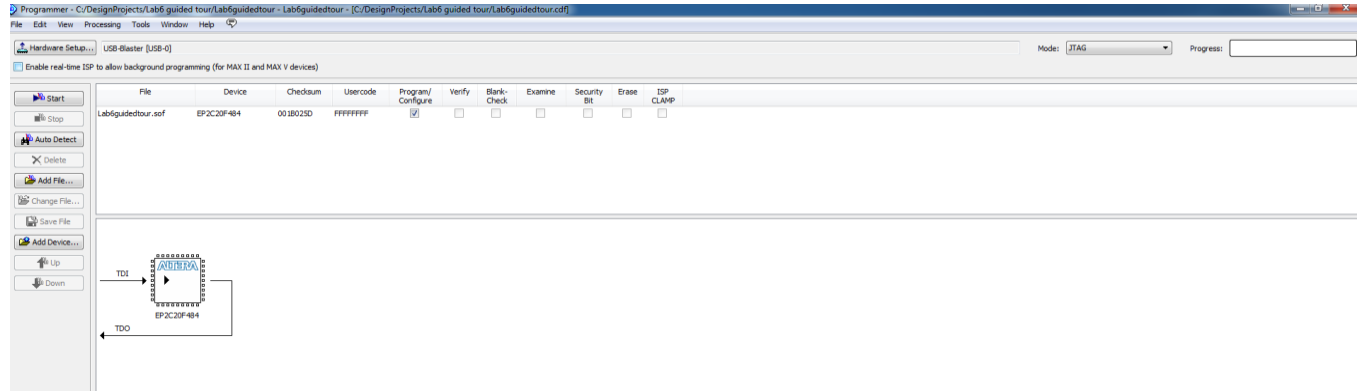5. Recompile your design to incorporate the pin assignments.
6. Program the Cyclone II with your design using the Quartus II Programmer tool as illustrated below. JTAG programming will be used, so make sure the RUN/PROG switch on the DE1 is still in the RUN position.

Begin programming by selecting **Tools > Programmer** from the Quartus II menu. This will display the following window.



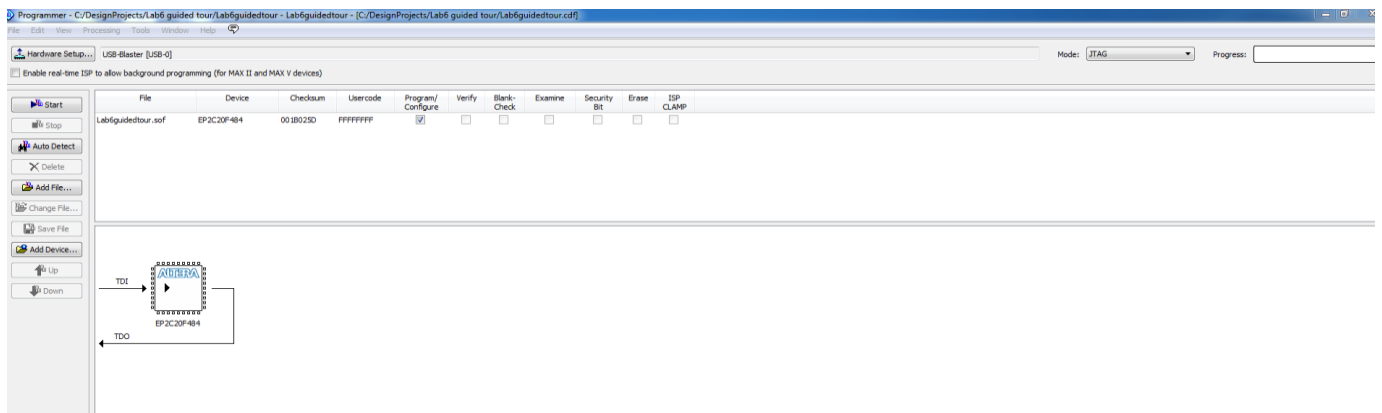Select **USB-Blaster** in the **Hardware Setup** box if it's not all ready selected. Make sure **JTAG** is selected in the **Mode** box. The window should look like this.



Now click the **Start** button to begin programming. The box will display 100% (Successful) when done. Programming will only take a few seconds.

The Cyclone II FPGA on the DE1 is now programmed with the design and testing can begin.

7. Exhaustively test your design on the DE-1 by successively entering the input patterns on SW3-SW0 and observing the responses on LEDG0.

A (SW3)	B (SW2)	C (SW1)	D (SW0)	f (LEDG0)
0 (down)	0 (down)	0 (down)	0 (down)	On/Off
0 (down)	0 (down)	0 (down)	1 (up)	On/Off
0 (down)	0 (down)	1 (up)	0 (down)	On/Off
0 (down)	0 (down)	1 (up)	1 (up)	On/Off
0 (down)	1 (up)	0 (down)	0 (down)	On/Off
0 (down)	1 (up)	0 (down)	1 (up)	On/Off
0 (down)	1 (up)	1 (up)	0 (down)	On/Off
0 (down)	1 (up)	1 (up)	1 (up)	On/Off
1 (up)	0 (down)	0 (down)	0 (down)	On/Off
1 (up)	0 (down)	0 (down)	1 (up)	On/Off
1 (up)	0 (down)	1 (up)	0 (down)	On/Off
1 (up)	0 (down)	1 (up)	1 (up)	On/Off
1 (up)	1 (up)	0 (down)	0 (down)	On/Off
1 (up)	1 (up)	0 (down)	1 (up)	On/Off
1 (up)	1 (up)	1 (up)	0 (down)	On/Off
1 (up)	1 (up)	1 (up)	1 (up)	On/Off

USING THE DE1 – DO-IT-YOURSELF EXERCISE

Implement and test the full-adder circuit that you designed in Laboratory 1 on the DE1 following the steps from the guided tour. Employ exhaustive testing. Use the following DE1 pin assignments. See Figure 3 for the pin-outs.

A (SW2) -> PIN_M22
 B (SW1) -> PIN_L21
 C (SW0) -> PIN_L22
 S (LEDG0) -> PIN_U22
 Cout (LEDG1) -> PIN_U21

Aout (LEDR2) -> PIN_U19
 Bout (LEDR1) -> PIN_R19
 Cout (LERD0) -> PIN_R20

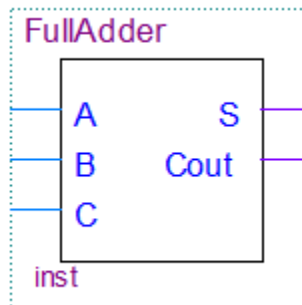


Figure 3. DE1 Do-It-Yourself Exercise Pin-Out Diagram.

IMPLEMENTING YOUR FOUR-BIT ADDER/SUBTRACTOR

Implement the Adder/Subtractor that you designed in Laboratory 3 on the DE1. Use the following DE1 pin assignments corresponding to the pin-out diagram in Figure 4.

AddSub (SW8) -> PIN_M1
 A3 (SW7) -> PIN_M2
 A2 (SW6) -> PIN_U11
 A1 (SW5) -> PIN_U12
 A0 (SW4) -> PIN_W12
 B3 (SW3) -> PIN_V12
 B2 (SW2) -> PIN_M22
 B1 (SW1) -> PIN_L21
 B0 (SW0) -> PIN_L22

AddSubout (LEDR8) -> PIN_R18
 A3out (LEDR7) -> PIN_U18
 A2out (LEDR6) -> PIN_Y18
 A1out (LEDR5) -> PIN_V19
 A0out (LEDR4) -> PIN_T18
 B3out (LEDR3) -> PIN_Y19
 B2out (LEDR2) -> PIN_U19
 B1out (LEDR1) -> PIN_R19
 B0out (LEDR0) -> PIN_R20

R3 (LEDG3) -> PIN_V21
 R2 (LEDG2) -> PIN_V22
 R1 (LEDG1) -> PIN_U21
 R0 (LEDG0) -> PIN_U22

Cout (LEDG7) -> PIN_Y21
 OVR (LEDG6) -> PIN_Y22

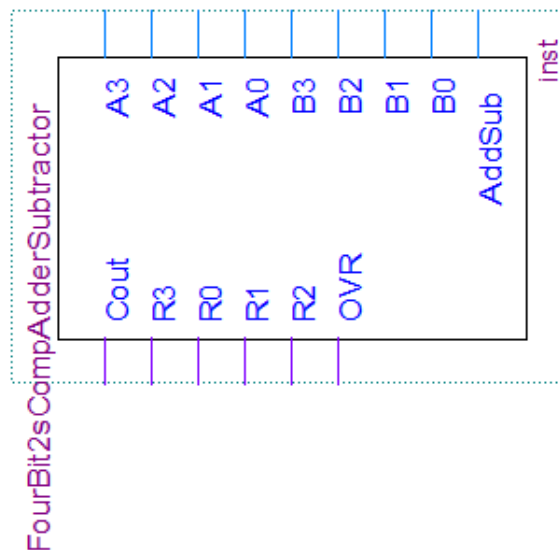


Figure 4. Four-Bit Adder/Subtractor Pin-Out Diagram

Test your implementation with the inputs given in the following table.

A	B	$R = A + B$	OVR	Cout(C4)	$R = A - B$	OVR	Cout(C4)
0101	0010						
0101	1110						
0101	0011						
1011	1110						
1101	1010						
1011	0000						

APPENDIX A – DE1 I/O Pin Assignments

<i>Input Switches</i>	<i>LED Outputs</i>	<i>Seven-Segment</i>
SW0 – PIN_L22	LEDR0 – PIN_R20	HEX0(0) – PIN_J2
SW1 – PIN_L21	LEDR1 – PIN_R19	HEX0(1) – PIN_J1
SW2 – PIN_M22	LEDR2 – PIN_U19	HEX0(2) – PIN_H2
SW3 – PIN_V12	LEDR3 – PIN_Y19	HEX0(3) – PIN_H1
SW4 – PIN_W12	LEDR4 – PIN_T18	HEX0(4) – PIN_F2
SW5 – PIN_U12	LEDR5 – PIN_V19	HEX0(5) – PIN_F1
SW6 – PIN_U11	LEDR6 – PIN_Y18	HEX0(6) – PIN_E2
SW7 – PIN_M2	LEDR7 – PIN_U18	
SW8 – PIN_M1	LEDR8 – PIN_R18	HEX1(0) – PIN_E1
SW9 – PIN_L2	LEDR9 – PIN_R17	HEX1(1) – PIN_H6
		HEX1(2) – PIN_H5
KEY0 – PIN_R22	LEDG0 – PIN_U22	HEX1(3) – PIN_H4
KEY1 – PIN_R21	LEDG1 – PIN_U21	HEX1(4) – PIN_G3
KEY2 – PIN_T22	LEDG2 – PIN_V22	HEX1(5) – PIN_D2
KEY3 – PIN_T21	LEDG3 – PIN_V21	HEX1(6) – PIN_D1
	LEDG4 – PIN_W22	
	LEDG5 – PIN_W21	HEX2(0) – PIN_G5
	LEDG6 – PIN_Y22	HEX2(1) – PIN_G6
	LEDG7 – PIN_Y21	HEX2(2) – PIN_C2
		HEX2(3) – PIN_C1
		HEX2(4) – PIN_E3
		HEX2(5) – PIN_E4
		HEX2(6) – PIN_D3
		HEX3(0) – PIN_F4
		HEX3(1) – PIN_D5
		HEX3(2) – PIN_D6
		HEX3(3) – PIN_J4
		HEX3(4) – PIN_L8
		HEX3(5) – PIN_F3
		HEX3(6) – PIN_D4